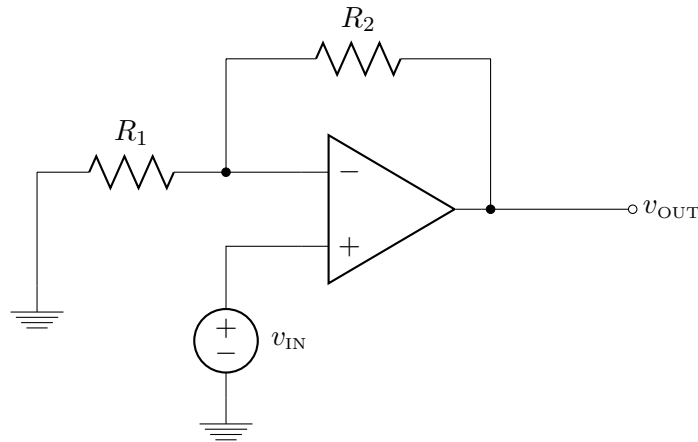


Problem 1. A non-inverting op amp configuration is shown below. The op amp has the following characteristics:

- DC open-loop gain  $A_0 = 40\text{dB}$ .
- Open-loop 3dB cut-off frequency  $f_c = 1\text{MHz}$ .
- Slew rate  $\text{SR} = 2\text{V}/\mu\text{s}$ .
- Rail voltages at  $\pm 5\text{V}$ .
- $R_1 = 1\text{k}\Omega$  and  $R_2 = 1\text{k}\Omega$ , so the ideal closed-loop gain is  $2\text{V}/\text{V}$ .





- Calculate the unity-gain frequency ( $f_t$ ) of this amplifier circuit. Give your answer in Hz.
- Calculate the 3dB cut-off frequency for the **closed-loop** circuit.
- Sketch the magnitude response (i.e. Bode plot) for this op amp, showing both the open-loop and closed-loop responses. Identify the unity-gain frequency.
- Calculate the full-power bandwidth (FPBW) for this op amp.
- If the circuit amplifies an input signal described by the equation

$$v_{\text{IN}} = V_{\text{IN}} \sin(2\pi ft),$$

answer these subquestions:

- If  $f = 1\text{MHz}$ , what is the maximum possible amplitude  $V_{\text{IN}}$  with no slewing?
  - If  $V_{\text{IN}} = 1\text{V}$ , what is the maximum possible  $f$  with no slewing?
- If  $v_{\text{IN}}$  is a square wave, is it possible to avoid slewing in the circuit's output?
  - Carefully study the axes and waveforms shown below. The waveforms are shown for the **ideal** behavior (with no slewing). If slewing is present, draw the resulting waveforms. You may assume that  $v_{\text{OUT}} = 0$  at time  $t = 0$ .

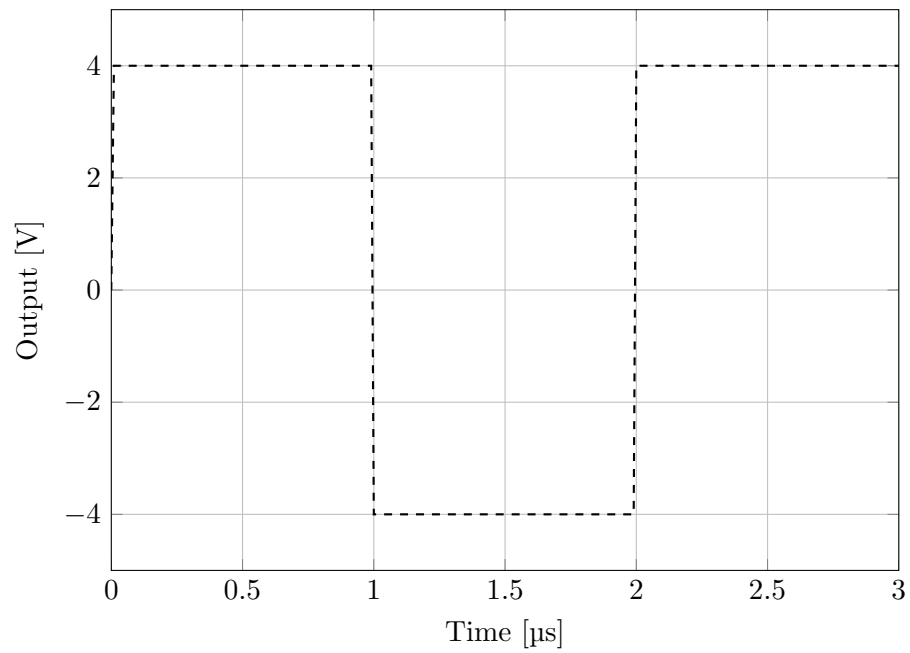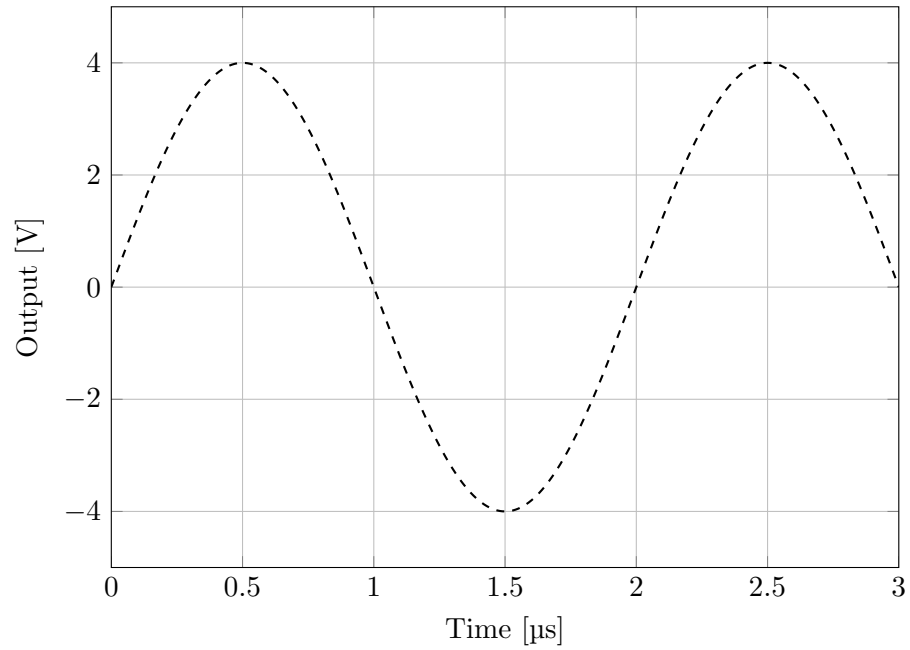


Problem 2. An inverting Miller integrator circuit is shown below. The component values are

$$R_1 = 10\text{k}\Omega$$

$$R_2 = 10\text{k}\Omega$$

$$C = 10\mu\text{F}$$

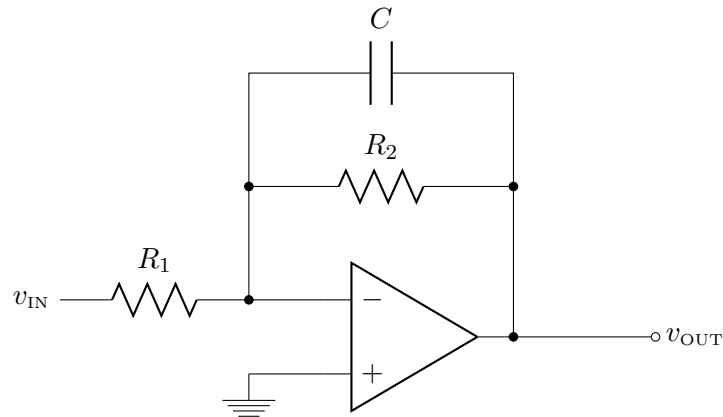

- (A) When operating at DC, the capacitor  $C$  can be viewed as an open circuit (i.e. as though it isn't there). What is the DC gain of this circuit?
- (B) Using Laplace-transform analysis, show that the steady-state transfer function is given by

$$H(s) = \left(-\frac{R_2}{R_1}\right) \left(\frac{1}{1 + sR_2C}\right).$$

You may assume that the op amp is ideal.

- (C) Since an integrator has transfer function of the form  $K/s$ , this circuit can only be considered an integrator for high-frequency signals. At low frequencies (close to DC), it is a unity-gain buffer. What is the cut-off frequency that separates the AC integrating mode from the DC buffering mode?
- (D) The magnitude response of a linear system is

$$|H(f)| = \sqrt{H(j2\pi f)H(-j2\pi f)}.$$

If the circuit has an input sine wave with amplitude 100mV at frequency  $f = 10\text{Hz}$ , predict the amplitude of the output waveform.

- (E) Suppose the op amp has an input bias current  $I_{\text{bias}} = 1\mu\text{A}$  and an offset voltage of  $V_{\text{ofs}} = 10\text{mV}$ . What is the resulting DC offset that appears at the circuit's output? (Remember that the offset voltage is modeled as a DC input applied to the op amp's non-inverting terminal).